

Write a VHDL code for 4:1 MUX using structural Modeling style

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Entity declaration for the 2-to-1 MUX
ENTITY mux2to1 IS
    PORT(
        a, b, sel : IN  std_logic;
        y        : OUT std_logic
    );
END mux2to1;

ARCHITECTURE behavior OF mux2to1 IS
BEGIN
    y <= a WHEN sel = '0' ELSE b;
END behavior;

-- Entity declaration for the 4-to-1 MUX
ENTITY mux4to1 IS
    PORT(
        d0, d1, d2, d3 : IN  std_logic;
        s0, s1        : IN  std_logic;
        y              : OUT std_logic
    );
END mux4to1;

ARCHITECTURE structural OF mux4to1 IS

    SIGNAL y0, y1 : std_logic; -- Internal signals

    COMPONENT mux2to1
        PORT(
            a, b, sel : IN  std_logic;
            y        : OUT std_logic
        );
    END COMPONENT;

BEGIN
    -- Instantiate the first level of 2-to-1 MUXes
    U1: mux2to1 PORT MAP (a => d0, b => d1, sel => s0, y => y0);
    U2: mux2to1 PORT MAP (a => d2, b => d3, sel => s0, y => y1);
    -- Instantiate the second level of 2-to-1 MUX
    U3: mux2to1 PORT MAP (a => y0, b => y1, sel => s1, y => y);

END structural;
```

Write a VHDL code for 8:1 MUX using structural Modeling style

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
-- Entity declaration for the 2-to-1 MUX
```

```
ENTITY mux2to1 IS
```

```
    PORT(
```

```
        a, b, sel : IN  std_logic;
```

```
        y        : OUT std_logic
```

```
    );
```

```
END mux2to1;
```

```
ARCHITECTURE behavior OF mux2to1 IS
```

```
BEGIN
```

```
    y <= a WHEN sel = '0' ELSE b;
```

```
END behavior;
```

```
-- Entity declaration for the 8-to-1 MUX
```

```
ENTITY mux8to1 IS
```

```
    PORT(
```

```
        d0, d1, d2, d3, d4, d5, d6, d7 : IN  std_logic;
```

```
        s0, s1, s2                      : IN  std_logic;
```

```
        y                              : OUT std_logic
```

```
    );
```

```
END mux8to1;
```

```
ARCHITECTURE structural OF mux8to1 IS
```

```
    SIGNAL y0, y1, y2, y3 : std_logic;
```

```
    SIGNAL y4, y5        : std_logic;
```

```
    COMPONENT mux2to1
```

```
        PORT(
```

```
            a, b, sel : IN  std_logic;
```

```
            y        : OUT std_logic
```

```
        );
```

```
    END COMPONENT;
```

```
BEGIN
```

```
-- Instantiate the first level of 2-to-1 MUXes
```

```
U1: mux2to1 PORT MAP (a => d0, b => d1, sel => s0, y => y0);
```

```
U2: mux2to1 PORT MAP (a => d2, b => d3, sel => s0, y => y1);
```

```
U3: mux2to1 PORT MAP (a => d4, b => d5, sel => s0, y => y2);
```

```
U4: mux2to1 PORT MAP (a => d6, b => d7, sel => s0, y => y3);
```

```

-- Instantiate the second level of 2-to-1 MUXes
U5: mux2to1 PORT MAP (a => y0, b => y1, sel => s1, y => y4);
U6: mux2to1 PORT MAP (a => y2, b => y3, sel => s1, y => y5);

-- Instantiate the third level of 2-to-1 MUX
U7: mux2to1 PORT MAP (a => y4, b => y5, sel => s2, y => y);

END structural;

```

VHDL code for an 8-to-1 multiplexer (MUX) using the behavioral modeling style

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux8to1 IS
    PORT(
        d0, d1, d2, d3, d4, d5, d6, d7 : IN  std_logic;
        s                               : IN  std_logic_vector(2 DOWNTO 0);
        y                               : OUT std_logic
    );
END mux8to1;

ARCHITECTURE behavior OF mux8to1 IS
BEGIN
    PROCESS(d0, d1, d2, d3, d4, d5, d6, d7, s)
    BEGIN
        CASE s IS
            WHEN "000" => y <= d0;
            WHEN "001" => y <= d1;
            WHEN "010" => y <= d2;
            WHEN "011" => y <= d3;
            WHEN "100" => y <= d4;
            WHEN "101" => y <= d5;
            WHEN "110" => y <= d6;
            WHEN "111" => y <= d7;
            WHEN OTHERS => y <= '0'; -- Default case
        END CASE;
    END PROCESS;
END behavior;

```

Write a VHDL code to simulate 1×8 Demultiplexer

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY demux1x8 IS
    PORT(
        d    : IN  std_logic;
        sel   : IN  std_logic_vector(2 DOWNTO 0);
        y0, y1, y2, y3, y4, y5, y6, y7 : OUT std_logic
    );
END demux1x8;

ARCHITECTURE behavior OF demux1x8 IS
BEGIN
    PROCESS(d, sel)
    BEGIN
        -- Default values
        y0 <= '0';
        y1 <= '0';
        y2 <= '0';
        y3 <= '0';
        y4 <= '0';
        y5 <= '0';
        y6 <= '0';
        y7 <= '0';

        CASE sel IS
            WHEN "000" => y0 <= d;
            WHEN "001" => y1 <= d;
            WHEN "010" => y2 <= d;
            WHEN "011" => y3 <= d;
            WHEN "100" => y4 <= d;
            WHEN "101" => y5 <= d;
            WHEN "110" => y6 <= d;
            WHEN "111" => y7 <= d;
            WHEN OTHERS =>
                y0 <= '0';
                y1 <= '0';
                y2 <= '0';
                y3 <= '0';
                y4 <= '0';
                y5 <= '0';
                y6 <= '0';
                y7 <= '0';
        END CASE;
    END PROCESS;
END demux1x8;
```

```
END PROCESS;  
END behavior;
```

VHDL program for which output will be 1 when the sequence 1101 is detected considering overlapping condition

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity sequence_detector is  
  port (  
    clk: in std_logic;      -- Clock input  
    reset: in std_logic;    -- Reset input  
    input_bit: in std_logic; -- Input bit stream  
    output_detected: out std_logic -- Output indicating sequence detection  
  );  
end entity sequence_detector;
```

```
architecture behavioral of sequence_detector is  
  -- Define states  
  type state_type is (A, B, C, D);  
  signal current_state, next_state: state_type;  
begin  
  process (clk, reset)  
  begin  
    if reset = '1' then  
      current_state <= A; -- Initial state  
    elsif rising_edge(clk) then  
      current_state <= next_state; -- State transition on clock edge  
    end if;  
  end process;
```

```
  process (current_state, input_bit)  
  begin  
    case current_state is  
      when A =>  
        if input_bit = '1' then  
          next_state <= B;  
        else  
          next_state <= A;  
        end if;  
  
      when B =>  
        if input_bit = '1' then
```

```

        next_state <= C;
    else
        next_state <= A;
    end if;

    when C =>
        if input_bit = '0' then
            next_state <= D;
        else
            next_state <= C;
        end if;

    when D =>
        if input_bit = '1' then
            next_state <= B; -- Detects "1101" and loops back to detect more occurrences
        else
            next_state <= A;
        end if;

    when others =>
        next_state <= A;
    end case;
end process;

-- Output assignment
process (current_state)
begin
    output_detected <= '0';
    case current_state is
        when D =>
            output_detected <= '1'; -- Output is '1' when "1101" sequence is detected
        when others =>
            output_detected <= '0';
        end case;
    end process;
end architecture behavioral;

```