
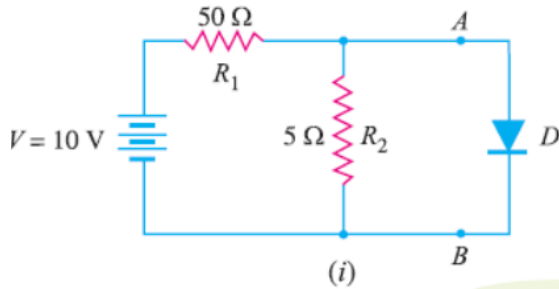


TUTORIALS 1

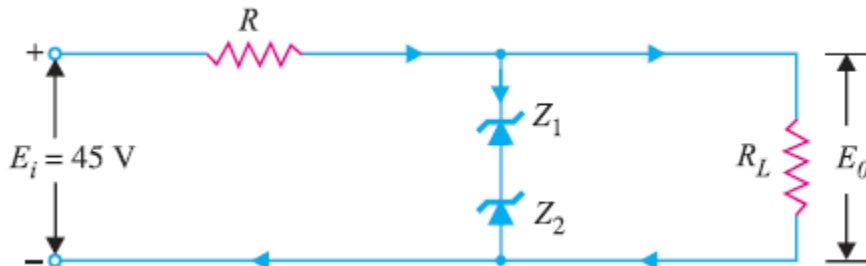
- Find the current through the diode in the circuit shown in Figure. Assume the diode to be ideal.



- A silicon diode has reverse saturation current of $2.5 \mu\text{A}$ at 300 K. Find forward voltage for a forward current of 10 mA.
- A silicon diode has a saturation current of 5nA at 25°C . What is the saturation current at 100°C .
- The circuit uses two Zener diodes, each rated at 15 V, 200 mA. If the circuit is connected to a 45-volt unregulated supply, determine : (i) The regulated output voltage (ii) The value of series resistance R.



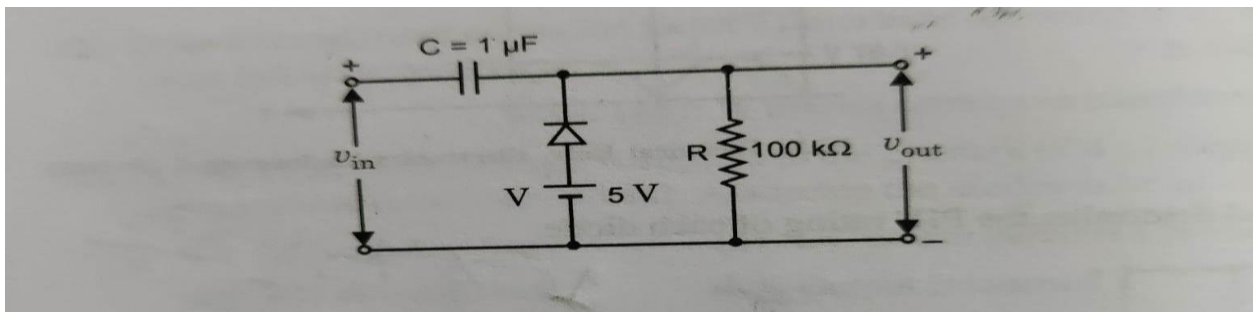- If input voltage is $15 \sin \omega t$ find the output waveform.



Example 5.9. A full-wave bridge rectifier uses $R_L = 2 \text{ k}\Omega$, each diode is to have forward resistance $R_F = 2 \Omega$ and $R_r = \infty$. A sinusoidal voltage having peak amplitude of 20 V is applied. Find out: (i) Peak, dc and rms values of load current; (ii) dc and rms output voltages; (iii) dc output power, (iv) ac input power, (v) efficiency.

-


7.

Example 5.9. A full-wave bridge rectifier use $R_L = 2 \text{ k}\Omega$, each diode is to have forward resistance $R_F = 2 \Omega$ and $R_r = \infty$. A sinusoidal voltage having peak amplitude of 20 V is applied. Find out: (i) Peak, dc and rms values of load current; (ii) dc and rms output voltages; (iii) dc output power, (iv) ac input power, (v) efficiency.


8.

Applications of Diodes

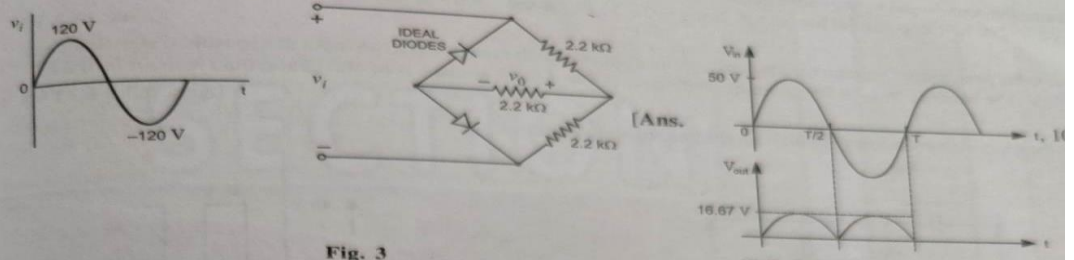
22. Sketch v_o for the network of Fig. 3.



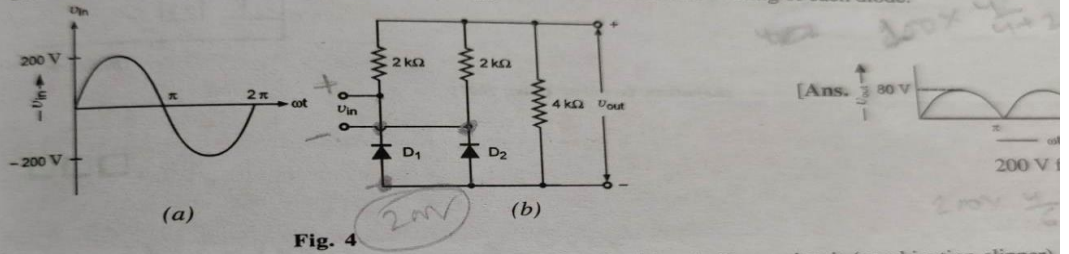
23. For the circuit shown in Fig. 4, sketch V_{out} and determine the PIV rating of each diode.



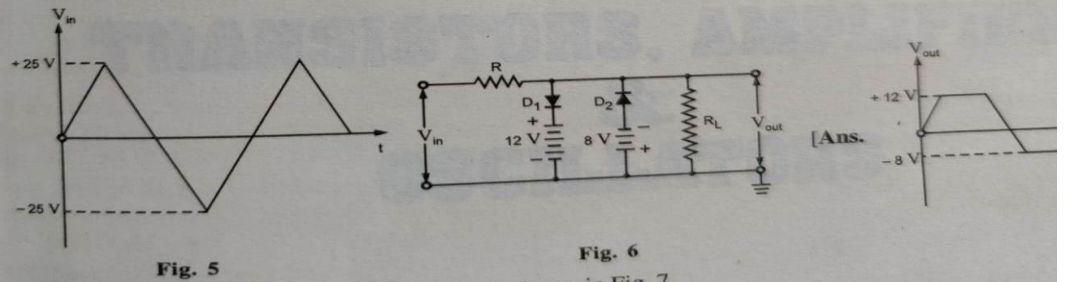
24. A triangular voltage shown in Fig. 5 is applied to the biased clipper circuit (combination clipper). Determine the wave-shape of the output voltage.



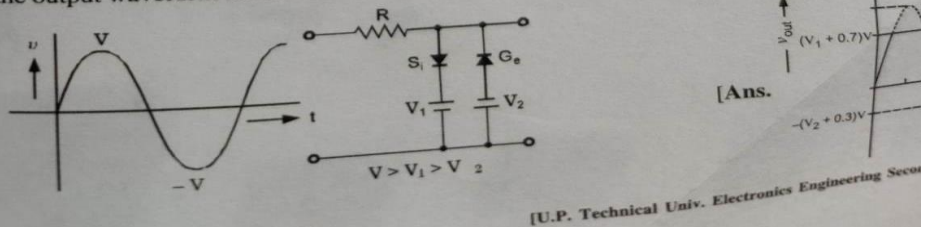25. Draw the output waveform for the circuit shown in Fig. 7.





9.

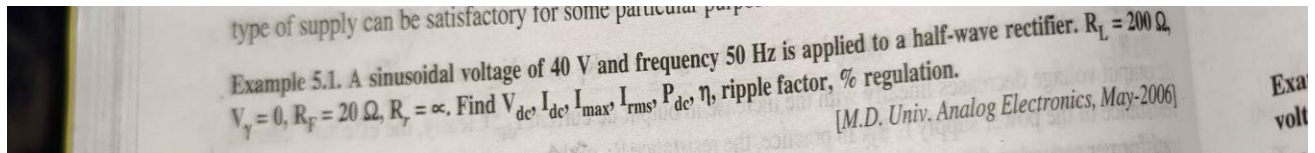

Draw a dc load line and find Q point for these circuits.


10.

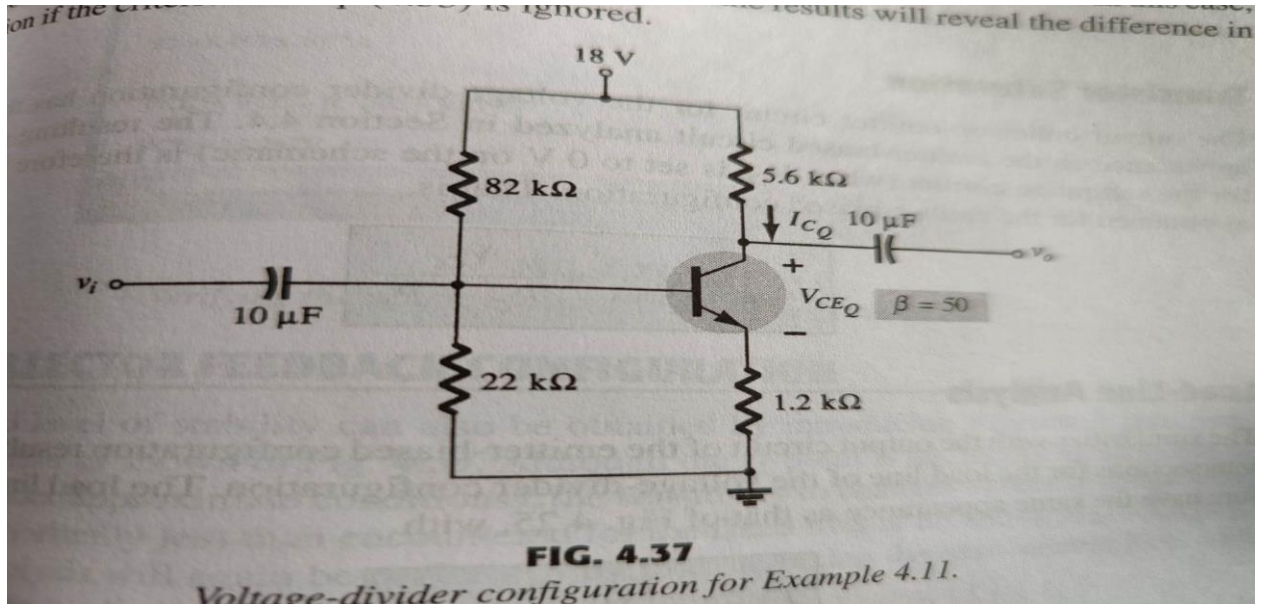

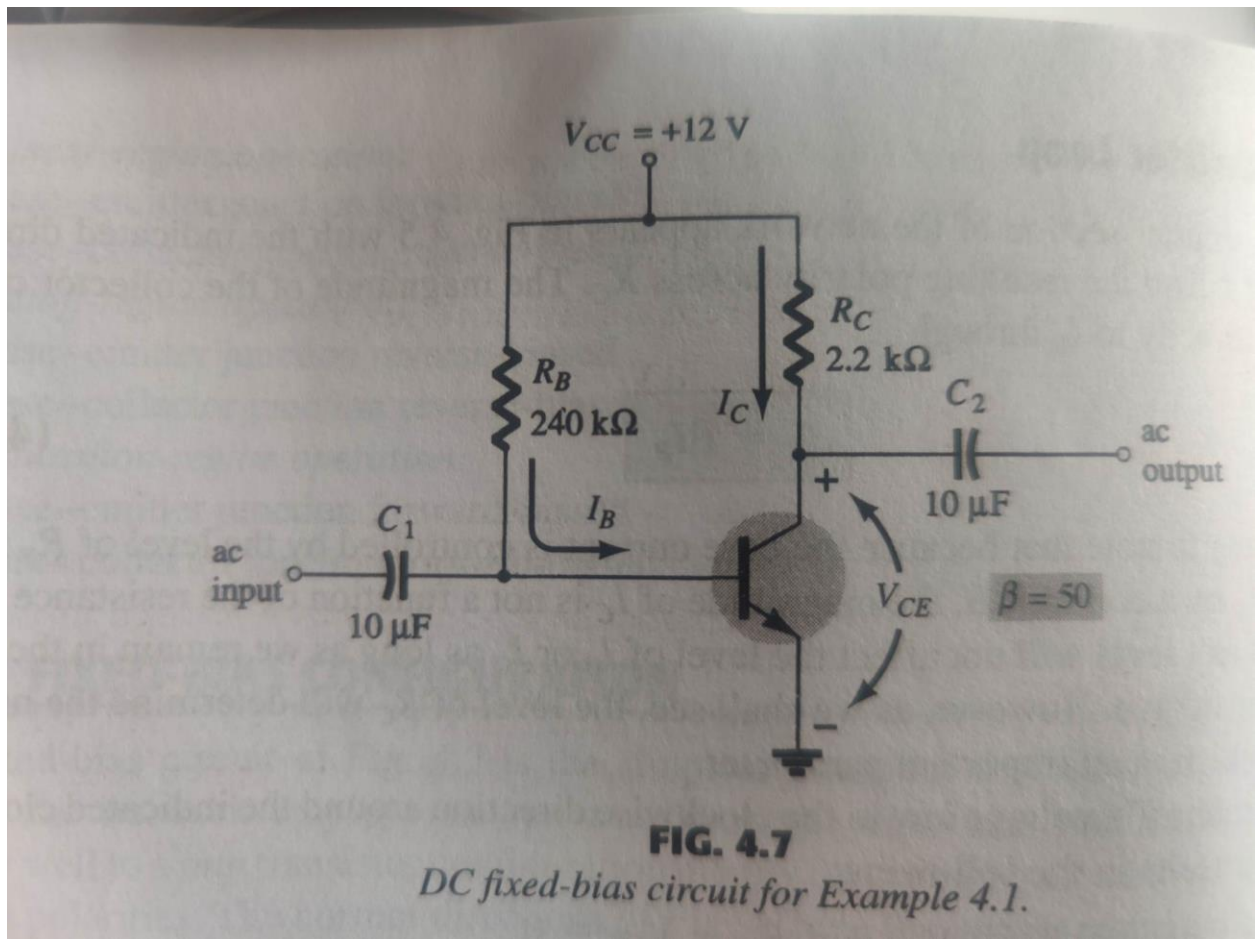

11.

12.

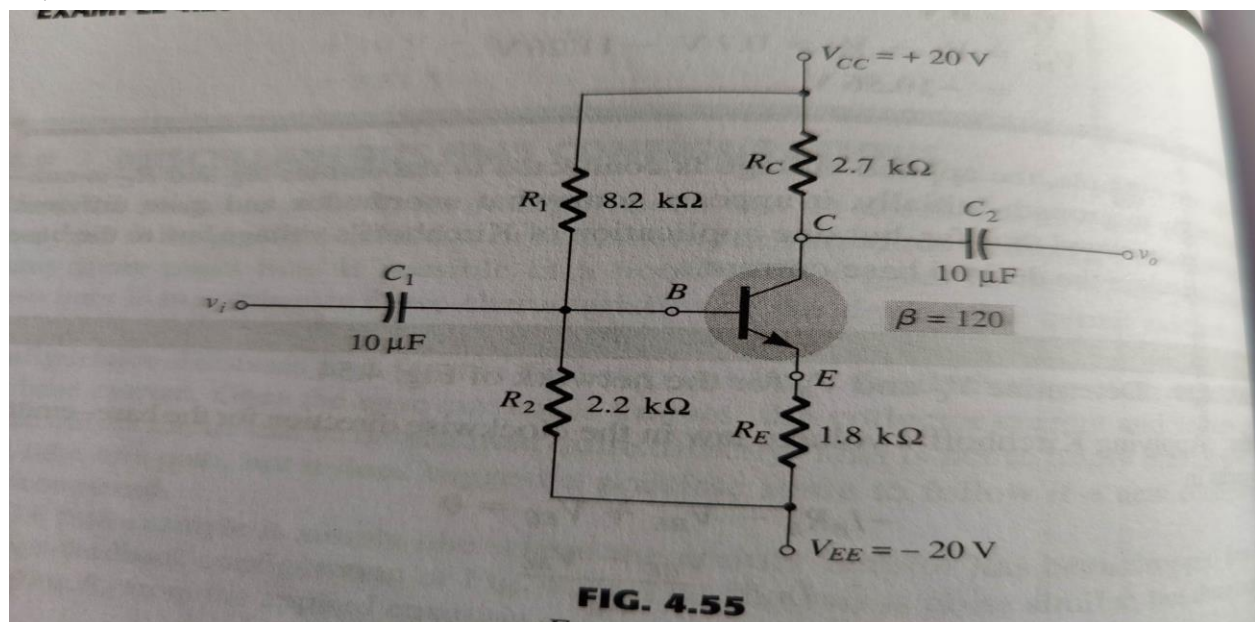

Base voltage, $V_B = V_{CC} - I_{BQ} R_B$

Example 7.6. Determine the resistor values for the following network (Fig. 7.11) for the indicated operating point and power supply voltage.

[U.P. Technical Univ. Electronics Engineering Second Semester 2006-07]

the operating point is


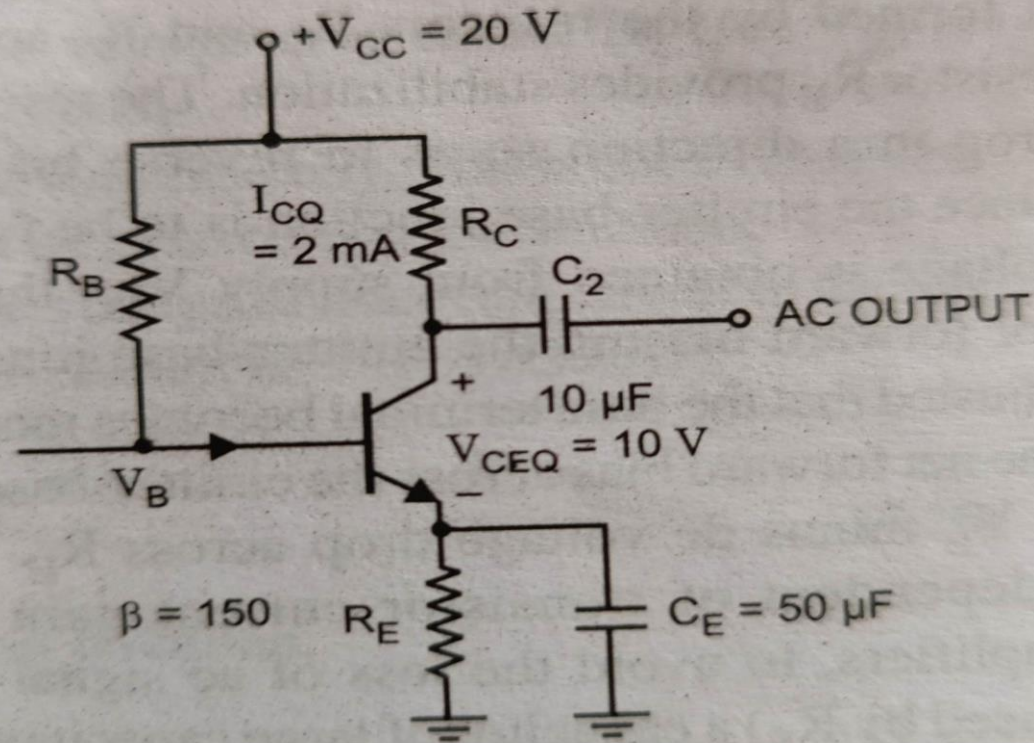


Fig. 7.11

EXAMPLE 5.20 For the network of Fig. 5.108, determine:

- Z_i
- Z_o
- A_v
- A_i

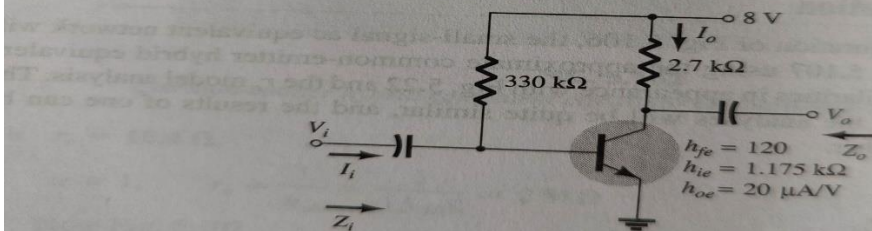

15.

EXAMPLE 7.1 Determine the following for the network of Fig. 7.6:

- V_{GSQ} .
- I_{DQ} .
- V_{DS} .
- V_D .
- V_G .
- V_S .

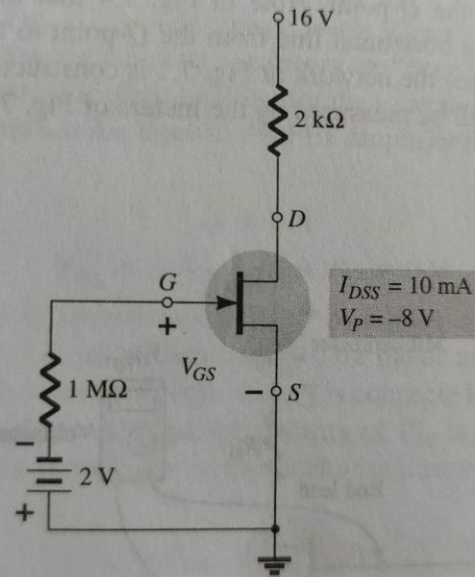


FIG. 7.6
Example 7.1.

16.

EXAMPLE 7.2 Determine the following for the network of Fig. 7.12:

- V_{GSQ}
- I_{DQ}
- V_{DS}
- V_S
- V_G
- V_D

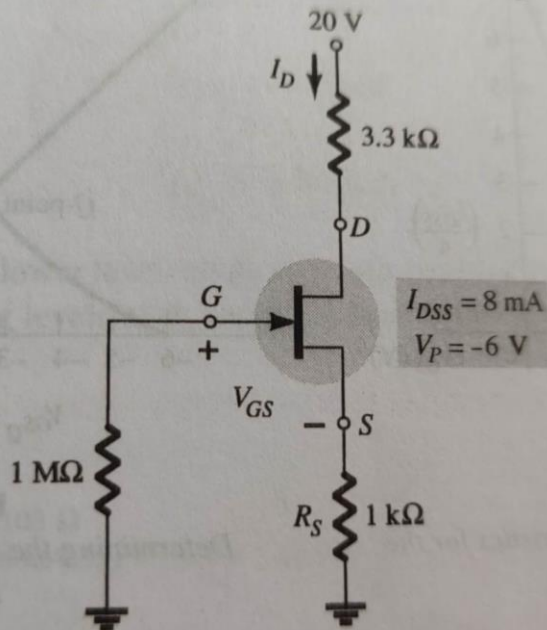


FIG. 7.12
Example 7.2.

17.

$$\text{or } V_{GS(\text{OFF})} = \frac{-2I_{DSS}}{g_{mo}} = \frac{-2 \times 10 \times 10^{-6}}{10 \times 10^{-3}} = -2 \text{ mV Ans.}$$

Example 9.9. An N-channel JFET has $I_{DSS} = 10 \text{ mA}$ and $V_P = -4 \text{ V}$. Determine the minimum value of V_{DS} for pinch-off region and drain current I_D for $V_{GS} = -2 \text{ V}$ in pinch-off region.

18.

EXAMPLE 5.19 Given $I_E = 2.5 \text{ mA}$, $h_{fe} = 140$, $h_{oe} = 20 \mu\text{S}$ (μmho), and $h_{ob} = 0.5 \mu\text{S}$, determine:

- The common-emitter hybrid equivalent circuit.
- The common-base r_e model.

19. 20

EXAMPLE 5.9 For the network of Fig. 5.62, determine:

- r_e .
- Z_i .
- Z_o .
- A_v .
- Repeat parts (b) through (d) with $r_o = 20 \text{ k}\Omega$ and compare results.

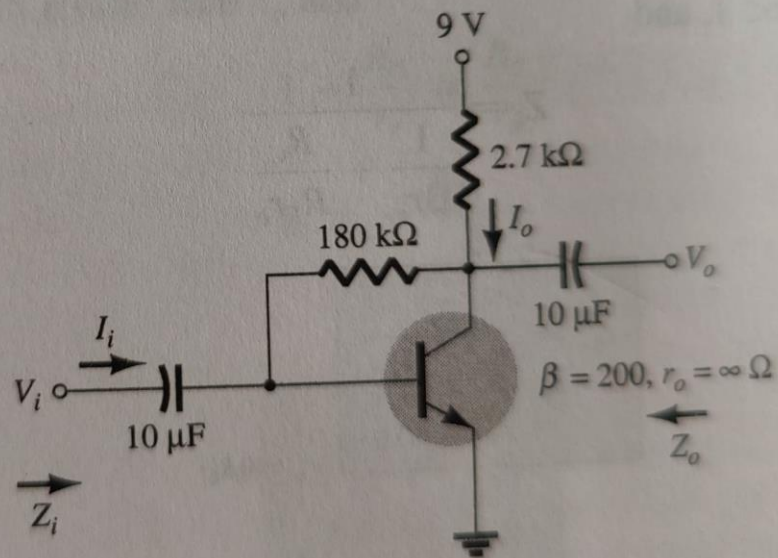


FIG. 5.49
Example 5.9.

20.


376

Basic Electronics

3. In a negative feedback amplifier $A = 100$; $\beta = 0.02$ and input signal voltage is 40 mV. Determine (i) voltage gain with feedback (ii) feedback factor, (iii) feedback voltage and (iv) output voltage.

[Ans. (i) 33.33 (ii) 2 (iii) 26.666 mV (iv) 1.333 V]

21.

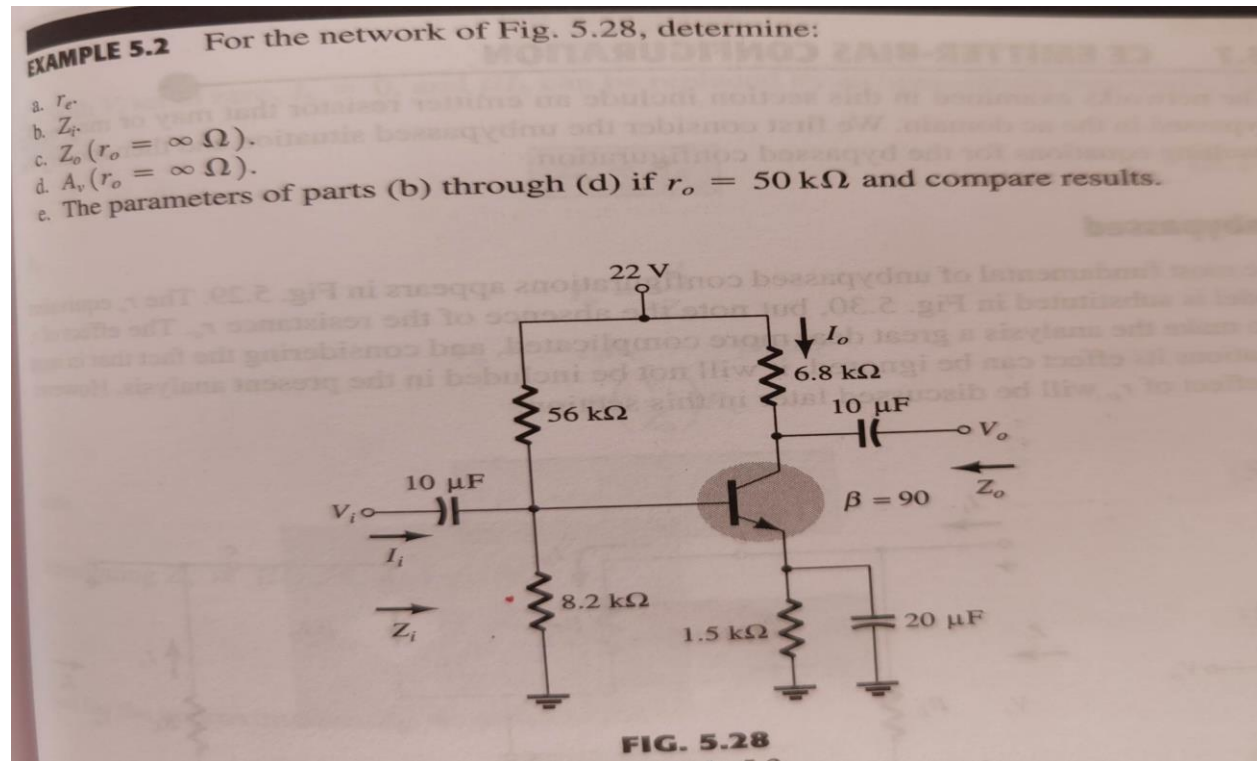

22.

376 Basic Electronics

3. In a negative feedback amplifier $A = 100$; $\beta = 0.02$ and input signal voltage is 40 mV. Determine (i) voltage gain with feedback (ii) feedback factor, (iii) feedback voltage and (iv) output voltage.

[Ans. (i) 33.33 (ii) 2 (iii) 26.666 mV (iv) 1.333 V]

23., 24

4. To an amplifier of 60 dB gain a feedback (negative) of $\beta = 0.006$ is applied. What would be the change in the overall gain of the feedback amplifier if the gain of the amplifier decreases by 15%. [Ans. 2.462%]

5. A single-stage amplifier has a voltage gain of 10 and a bandwidth of 1 MHz. Three such stages are cascaded and a negative feed of 10% is applied to the cascade stage. Find the overall voltage gain and bandwidth of the cascaded stage with feedback. [Ans. 10; 100 MHz]

6. The resonant circuit of a tuned-collector transistor oscillator has a resonant frequency of 10 MHz. If the value of

25, 26, 27.


Capacitance is increased by 40%, calculate the new resonant frequency.

7. Determine the operating frequency of a Colpitt's oscillator shown in Fig. 11.14 if $L = 50 \mu\text{H}$, $L_{\text{RFC}} = 0.8 \text{ mH}$, $C_1 = 0.01 \mu\text{F}$, $C_2 = 0.02 \mu\text{F}$, $C_C = 20 \mu\text{F}$. [Ans. 275 kHz]


8. Determine the oscillation frequency of a transistor Hartley oscillator shown in Fig. 11.16 with circuit values $L_1 = 150 \mu\text{H}$, $L_2 = 1.5 \text{ mH}$, $M = 75 \mu\text{H}$ and $C = 150 \text{ pF}$. [Ans. 306 kHz]

9. In a Wien bridge oscillator shown in Fig. 11.23 if $R_1 = R_2 = 110 \text{ k}\Omega$ and $C_1 = C_2 = 1,600 \text{ pF}$. Determine frequency of oscillation. [Ans. 904 Hz]

28.

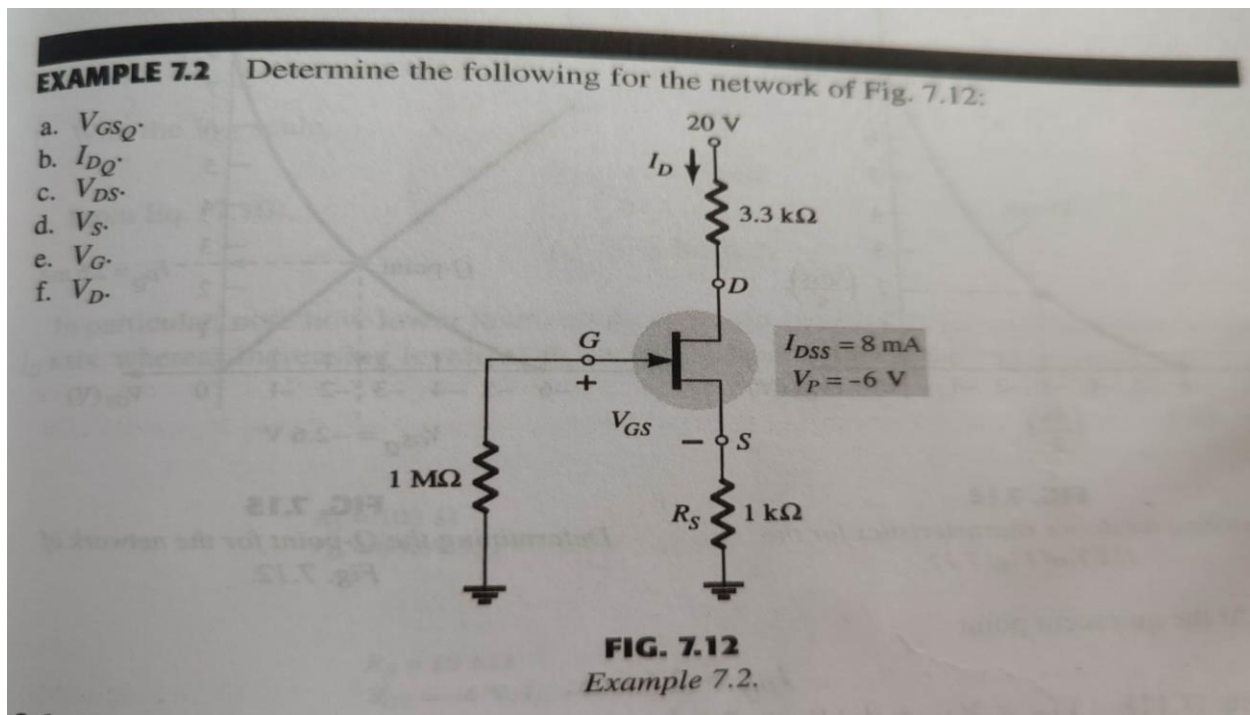

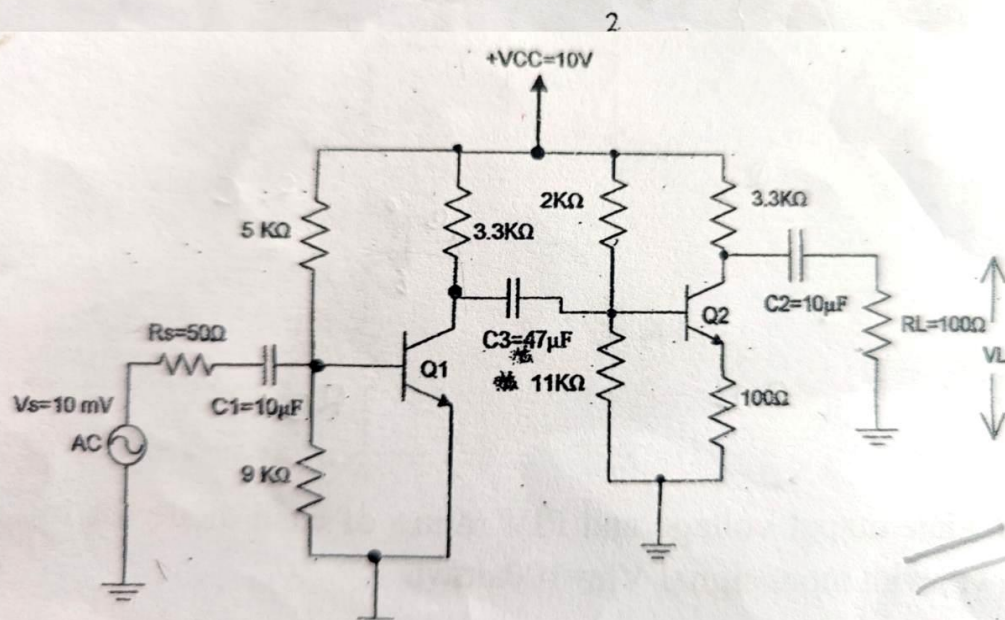b) Find V_1/V_S in the circuit below: ($\beta_1 = \beta_2 = 100$, $r_{e1} = r_{e2} = 25 \Omega$).



29.